 


Moore vs. Mealy FSM


- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last four digits it has crawled over are 1101. Design Moore and Mealy FSMs of the snail's brain.



155

ARM

Moore FSM in Verilog

 

```

module moore_snail(input  clk, reset,
                  bnum,
                  output reg smile);

    reg [2:0] state, nextstate;

    parameter S0 = 3'b000;
    parameter S1 = 3'b001;
    parameter S2 = 3'b010;
    parameter S3 = 3'b011;
    parameter S4 = 3'b100;

    parameter delay = 1;

    // state register
    always @(posedge reset, posedge clk)
    begin
        if (reset) #delay state <= S0;
        else #delay state <=
            nextstate;
    end

```

```

// Next State Logic
always @(*)
begin
    case (state)
        S0: if (bnum) #delay nextstate <= S1;
            else #delay nextstate <= S0;

        S1: if (bnum) #delay nextstate <= S2;
            else #delay nextstate <= S0;

        S2: if (bnum) #delay nextstate <= S2;
            else #delay nextstate <= S3;

        S3: if (bnum) #delay nextstate <= S4;
            else #delay nextstate <= S0;

        S4: if (bnum) #delay nextstate <= S2;
            else #delay nextstate <= S0;

        default: #delay nextstate <= S0;
    endcase
end

// Output Logic
always @(*)
begin
    if (state == S4) smile <= 1'b1 ;
    else smile <= 1'b0 ;
end
endmodule


```

156

ARM

Mealy FSM in Verilog

Mealy FSM: arcs indicate input/output

 

```

module mealy_snail(input      clk,
                  reset, bnum,
                  output reg  smile);

  reg [1:0] state, nextstate;

  parameter S0 = 2'b00;
  parameter S1 = 2'b01;
  parameter S2 = 2'b10;
  parameter S3 = 2'b11;

  parameter delay = 1;

  // state register
  always @(posedge reset, posedge clk)
  begin
    if (reset) #delay state <= S0;
    else       #delay state <=
nextstate;
  end

```

```

// Next State and Output Logic
always @(*)
begin
  case (state)
    S0: begin
      #delay smile <= 1'b0;
      if (bnum) #delay nextstate <= S1;
      else     #delay nextstate <= S0;
    end

    S1: begin
      #delay smile <= 1'b0;
      if (bnum) #delay nextstate <= S2;
      else     #delay nextstate <= S0;
    end

    S2: begin
      #delay smile <= 1'b0;
      if (bnum) #delay nextstate <= S2;
      else     #delay nextstate <= S0;
    end

    S3: begin
      if (bnum) #delay smile <= 1'b1;
      else     #delay smile <= 1'b0;
      if (bnum) #delay nextstate <= S1;
      else     #delay nextstate <= S0;
    end

    default: begin
      #delay smile <= 1'b0;
      #delay nextstate <= S0;
    end
  endcase
end
endmodule

```

157

ARM

Testbench for Snail FSM

```

`timescale 1ns/1ps

module fsm_snail_tb( );
  reg clk, reset, bnum;
  wire smile_moore;
  wire smile_mealy;

  parameter clk_period = 10;

  moore_snail moore_snail_uut
    (clk, reset, bnum,
     smile_moore);

  mealy_snail mealy_snail_uut
    (clk, reset, bnum,
     smile_mealy);

  initial
  begin
    reset = 1;
    #13
    reset = 0;
  end

  always
  begin
    clk = 1;
    forever #(clk_period/2) clk =
~clk;
  end

```

```

  initial
  begin
    bnum = 0; #3;
    bnum = 0; #clk_period;
    bnum = 1; #clk_period;
    bnum = 0; #clk_period;
    bnum = 0; #clk_period;
    bnum = 0; #clk_period;
    bnum = 1; #clk_period;
    bnum = 1; #clk_period;
    bnum = 0; #clk_period; // Smile
    bnum = 1; #clk_period;
    bnum = 0; #clk_period;
    bnum = 1; #clk_period; // Smile
    bnum = 0;
  end
endmodule

```

158

ARM